| Topic:   | Date:   |
|--|---|
| <u>Current</u> Electricity<br>→ Current · Rate of flow of charges.           | Current   |
| <u>T</u> = <u>Q</u> Charge<br>Current <u>E</u> time.                         | (Thomas Edison) (Nikola testa<br>Direct Current Alternating Current<br>* Current Flows in * Direction of current<br>one direction changes many time |
| Current depends on 2 things  | * Battery 11 in a second  |
| -> quantity of charge<br>-> Speed of flow.                                   | * Cell   * AC supply -0 0-<br>* DC supply -0 0-   |
| Current<br>Conventional<br>Electron flow                                     | Comection of<br>battery is<br>reversed.   |
| Current  | Voltage: Strength of Electricity.   |
|  | Energy that a coulomb charge has in a circuit.  |
| Conventional current Electrons flow from<br>is concidered to -ve terminal to |   |
| more trum the to the terminal.<br>-ve  |   |

Othmis Row: V~I Non Ohmic Conductor Voltage is directly proportional to 1) Thermistor as temperature Current provided that Area increases Resistance decreases. and temperature remains constant.  $\mathbf{V}$ Resistance: Ratio of Voltage - Current ß  $R = \frac{V}{T}$ Ohmic conductor Since Ratio of V decreases. T R = constant Resistance decreases. Ratio of \* Never use term gradient decreases V-T. remains I. constant. > [ 1) Fixed resistor 2) All metals Constant temperature Since Ratio of I/V increases. therefore ratio & V decreases here resistance decreases.  $\frac{R = V}{T} \frac{I}{V} \frac{R}{R}$ 

Date:

2) Filament lamp : As temperature 3) Diode -, Cathode. increases Resistance increase V anode . B Forward biased = IF offers a very low Resistance. <u>Y</u> increase hence : Current flows. As ratio of resistance increase T Reverse biosed It offers infinite Resistance. . No current flows Since ratio of <u>I</u> decreases hence IN robo is increases ratio of V increase hence henre V/T decreases. resistance increases -~ **I**=0 Forward biased. Reverse biesed

Topic:

Date:

R Min D Conductivity: 3t is Ex 4 ٢. the inverse of Resistivity R Max RA (\_\_\_\_)  $\sigma = \int f^{-1}m^{-1}$ -> A wire offers a resistance of \* I/1 resistance Minimum 10 r colculate the resistance of \* V A Resistance Maximum. the wire when the length is doubled and volume remains un changed.  $R = \frac{fl(2)}{A}$   $V = \frac{l \times B \times W}{2}$   $\frac{2l}{x} = \frac{2}{y}$   $\frac{1}{y}$   $\frac{1}{y}$ Factors Affecting Resistance.  $R \propto \frac{1}{A} R \propto kl$ Constant (21) × A 2) Ral R = (ypl) P 1 J = Resistivity. 402 1 x m SI unit = \_\_\_\_m R = Pl A ρ (d) \* Resistivity of the material is Er 2 Soid to be equal to its resistance 2L provided that material is of N unit length and offer a unit Cross sectional orea. <u>R=P1</u> 0 28 Both made &  $\mathcal{S} = \frac{RA}{\rho}$ Some moterial Calculate of IP b) VP

Topic: Date: \_ Current: Rate of Flow of  $Rp = \frac{f^2 2k}{f^2}$ 2 charge. Rg= Slk T = Q Q = TtRp~  $I_{P_{-}}(1)$ unit = A or C/s Τq, Q = It This can only be used when current remains b) In Pardlel voltage remain, some En3 Copper Steel Constant IF current is not constant \_\_\_\_2L R - 3R  $\Rightarrow \frac{P}{Colculate} + \frac{2P}{diameter} + \frac{dc}{dc}$  $Q = I_{Avg} \times t$ d s steel Copper - diameter of Q) A Current of 200mA flows 85 colculate charge. For  $= R = \frac{2P.l}{\pi c \partial t^2}$  $3R = \frac{f \cdot 2l}{\pi d \cdot 2}$ Q = 200 x 8  $\frac{3\left(2^{\beta}l\right)}{\pi ds^{2}}$ - 1600 mC  $= \int 2R$  $\pi d_{c^{2}}$ O) A current uniformely increases from 200mA to 1000mA in  $\frac{3}{dt^2} =$  $\frac{1}{dc^2}$ 12s.  $Q = 2.00 + 1000 \times 12$  $\frac{dc^{x}}{dc^{x}}$ 2 600 × 12 > 7200 mC 🤮 🗍 🛇 0309 2656780 💿 mahad\_\_amer 🛛 mahadamerchaudhry@gmail.com

Topic: \_\_\_\_\_ Date: \_\_\_\_ ⇒Concept of Prift velocity: Voltage Amount of workdone in moving a unit charge through the external circuit.  $\begin{array}{c} A \end{array} \left( \begin{array}{c} & \swarrow^{e} & \swarrow^{e} \\ & \swarrow^{e} & \swarrow^{e} \end{array} \right) \\ & \swarrow^{e} & \swarrow^{e} \end{array} \right)$ V = M M = qVVolte V or J/c Power (Electrical) When no potential difference is applied the electrons move in the conductor moves completly  $\frac{P = VI}{P = I^2 R} = \frac{P = V^2}{R}$ generated , Powerlaw, R randomly. Such that the net Current flowing through the conductor developed , Power dessignated is zero Amperes. - produced When the ends of the conductor, Electrical Energy ore connected to the power supply Battery creates a electric field E = Pt this electric field causes electrons  $\mathcal{E} = VIT$   $\mathcal{E} = I^2 R t$   $\mathcal{E} = \frac{V^2}{R} t$ to start moving in one direction generated , Powerloss as a result flow of current developed , Power dessignated occurs. the speed with which \_\_\_\_\_ produced the electron now move through the conductor is referred be as the drift velocity of "electrons." V=mean duft velocity: the average speed of the charged porticles. when there is a current in the conductor

|   | 2 | to |  |
|---|---|----|--|
|   | d | ιe |  |
| - | ~ | ~~ |  |

| Concept of Drift velocity      |                                  |
|--------------------------------|----------------------------------|
|                                | Length = L                       |
|                                | Area = A                         |
| I current                      | charge on electron = e           |
|                                | drift velocity - v               |
| → I1 ~ 3                       | n = no of electrons              |
| Show that Current I in this    | Present in 1m? of                |
| Conductor can be given by      | this conductor                   |
| this equation $T = n A v e$    | (number of electrons per)        |
|                                | Unit Volume                      |
| 1) 1m <sup>2</sup> n electrons |                                  |
| AL AL electrons.               | I = n Ave.                       |
|                                |                                  |
| 2 lelectron Charge → (e)       |                                  |
| hAl electrons - Ale            | = no of electrons depends on the |
|                                | conductor if good conductor n is |
| 3 Current = Total charge       | high and bad conductor           |
| time                           | n is low.                        |
|                                |                                  |
| I - "Alle                      | $V = \overline{\bot}$            |
|                                | n Ac                             |
| I = n Ave.                     |                                  |
|                                |                                  |
| v = velocity V copital thats   |                                  |
| Voltage.                       |                                  |
| •<br>•                         |                                  |
|                                |                                  |

Topic:



| - |   |    |  |
|---|---|----|--|
| 0 | n | 0  |  |
| U |   | C. |  |

Date:\_\_\_\_\_

| Compare Drift velocity in a   | Compare drift velocity in  |
|---|--|
| parallel Combination.   | Series and parallel circuits.  |
| $P = 2P, d, 3L, n = A$ $Q = 3P, 3d, 2L, 2n = QA$ $i) = R_{p} = ii = I_{p}$ $K_{p} = I_{p} = I_{p}$  | Resister length diameter Area<br>P<br>L<br>2<br>2<br>2<br>2<br>2<br>2<br>2<br>2<br>2<br>4<br>2<br>2<br>2<br>2<br>2<br>2<br>2<br>2<br>2<br>2<br>2<br>2<br>2 |
|   | R L 3L   |
| i) 28.31  |  |
| $ \rightarrow 9 $   | + P, Q and R made of same  |
| $\frac{3P \cdot 2P}{9P} \qquad \frac{1}{P} \qquad \frac{1}{P}$ | i <u>) Rp</u> ii) <u>Ip</u><br>Rg Io   |
| $\frac{1}{\frac{1}{\sqrt{q}}} \frac{1}{\frac{1}{\sqrt{q}}} \frac{1}{\sqrt{q}} \frac{1}{q$  | iii) <u>Va</u><br>V <sub>R</sub>   |
| 2   |  |

| Topic:                             | Date:   |
|------------------------------------|---|
| Case 5: Compare drift velocity     | * Compare drift velocity in Z with                    |
| in a series circuit whose          | drift velocity in x =?                                |
| resichance is channel              | T C   |
| registion le 15 Chiangeou          |   |
|                                    | п пс  |
|                                    | ΑζΤ   |
|                                    | $V_2 = \frac{0.11}{100000000000000000000000000000000$ |
| × Y ×                              |   |
|                                    |   |
| 2-6 0-6 2-6                        | n1A/  |
|                                    | $\frac{\partial \cdot SI}{\partial \cdot 2(1)}$       |
|                                    | T   |
| But Put of a state                 | A   |
| Doth hebistors & are replaced with |   |
| two identical Resistors Z mode of  |   |
| Some material as x but having      | <u> </u>  |
| half the diameter Calculate        | <u> </u>  |
| new vidue of current               | 42 7.9  |
| Area a l                           | <u>×</u>  |
| 4                                  |   |
| Kesistane *4                       | * Ezplain how drift velocity in                       |
|                                    | Z compares with drift velocity                        |
|                                    | ofx   |
|                                    | T = half . Area = gyater                              |
| X Y X                              |   |
|                                    | * We con say that change in                           |
|                                    | Area out weighs the change in                         |
| Current:                           | current   |
|                                    | V « As area 7   |
|                                    | A   |
|                                    |   |
|                                    | decreases drift velocity increases.                   |
| O TO 0700 2050700 @ mahad amor     | mahadamarchaudhru@gmail.com                           |

shauun ywyman. ື ILIEI

Topic: Date: ⇒ How to calculate efficiency iv) Efficiency of Circuit in Electrical Circuits. Useful voltage 100 heater Total voltage P = 1200W V = 240V 240 x 100 =7 280 P=VE 4 Leach 1200 = I N) How to increase efficiency. i) Calculate the current supplied to 1) By using wires with more diameter. the heater  $\rho = V \Sigma$ 2) Use wire of good conductor <u>1200 \_ I</u> I = 5A 240 ii) Calculate the voltage across both the connecting wires V = IRV = 5A (41) 20 V \* Each wire ubilizes 201 hence 40v voltage is masted. iii) Calculate the voltage Supplied by the power supply for the heater to operate at its normal Copocify 240 + 20 + 20 = 280v

Topic: Date: 2) Potential divider circuit Comparing b/w a variable resistor Circuit and a potential divider circuit. 1) Variable Resistor Circuit. R A 6 1 n-18-N 121 i) Colculate the current when i) Calculate minimum current in sliding contact is placed at the bulk V=IR  $\mathcal{I} = \frac{V}{R}$ B, Bulb get 12V;  $R = 6 \Omega$  $\mathbf{I} = \underline{12} \quad \mathbf{0.5A}$ 24 B => V = 12 ii) Calculate maximum current in  $\frac{T = 12}{2} = 2A$ the bulb. |||-|2 V T = 12 ii) Calculate the current in the 2A bull when sliding contact 6 is at A.  $A \Rightarrow V = 0$ 0.5 < I < 2A T = 0 OABoth circuit can be used to adjust brightness but Potential divider gives VO&I < 2A wide range and you can switchit df.

Topic: Date: 64 Concept of External Resistor R  $\rightarrow v = 2v$ Lost internal resistor r Voltage V potential drop V Electromotive force E 20 4V => Terminal potential External Resistor (R) : Resistance V = IR Difference V of any component appliance connected or Voltage or in the circuit PD Internal Resistance(r) : Resistance ) Colculate Current Supplied? offered by the chemicals inside V = IR the battery to the flow of current 6V = T3Л OLD Exems VS New Exems T = 2A Voltage/PD/Termind Potenbid difference: R Amount of Electrical Energy Converted into other forms when a unit charge flows through the external Circuit Lost volts (v): The energy dissopated or lost in the form of heat when a unit charge Flows through the internal resistance/internal circuit. Pot enticl 🖂 mahadamerchaudhry@gmail.com 🤮 🗍 🛇 0309 2656780 🞯 mahad\_\_amer

Date: \_\_\_\_\_ Topic: EMF (Electromolive Force) Terminal Potential Difference Sum of terminal potential difference (V) and lost volts (v) V=IR is EMF EMF = V + vLost Volts/ Potenic Orop Defination It is defined as v=Ir the amount of chemical energy converted into Electrical forms EMIF when a unit charge flows through a complete circuit EMF = V + V Plot graph of V against  $EMF = IR + I_r$   $EMF = I(R_{+r})$ EMF  $(\mathcal{E})$ E = V + yE = V + Tr $\xi - \overline{L}_{\ell} = V$ -1 E = V + vT E = V + v $E = V + I_r$ \* Straight line graph  $E = V + T_r$ V = E - Lrwith negative gradient V = E \_ Ir and a positive V = -rI + EV = -rT + Ey intercept.  $\gamma = m \varkappa + C$ 

Topic: \_\_\_\_\_ Date:\_\_\_\_\_ Worked Example: V 4 7 Â  $\overline{7}_{\Gamma}$ 2 1) Colculate E Variable Resistor \_ii) Y \_/ iii) Sketch a new graph where E=halved r= doubled Q) When V.R is set at R, i)  $\mathcal{E} = 4 \gamma^{\mu}$ Voltmeter reads IV and ii)  $r = 2_{-1}$ Ammeter reads 0.25A When VR is set at R2, iii) Voltmeter reads 0.9% and Ч-Ammeter reads 0.3A 2 1) Calculate R. R2, E, r 0.5 2  $iii) E = V + I_r$ i)  $V = IR_{\mu}$ <u>R = V</u> T <u>4\_2 = 2</u>  $1 = 0.15 R_{1}$ E = 1 + (0.25)(r) - 0Г 4\_2 = R, E = 0.9 + (0.3)(r) -2 0.5A ii)  $V = IR_2$  $0.9 = R_2$ \_\_ ۲ = ۲ 0.3 E = 1.5V  $3 = R_2$ 

Topic: Date: How to charge an uncharged => How can we determine weather battery using a power source or not a battery had internal Primay cell Power source Resistance and how to calculate cherling ~ its volue. 210 T 3·4\_L 7 EMF (v) Connecting J-2.0 VEI Wites . Seconday cell Battey that needs lost volts = 1V to be charged. i) Calculate Charging current V = IR J- difference 20-12 = I (0.5+0.1+3.4) I = 2AFor Ideal battery lost rolts - Or ii) Colculate Power supplied by Primory cell.  $\rho = VI$ P = 20(2)40 Watt iii) Calculate Power dissapated in the circuit.  $P = I^2 R$  $P = (2)^{2} (0.1 + 3.4 + 0.5)$ = 16 W

Topic: Date: in) Calculate He efficiency Resistors in Parallel E = 24 x 100 40 3.1 E = 60 r. efficient.  $\frac{1}{R_1} \neq \frac{1}{R_2}$ h R.  $= \frac{1}{6} + \frac{1}{3}$ -Properties of Resistors in Series and Parallel.  $R_{\tau} = 2 \Omega$ you have 2 resistors 1F 4\_<u>1</u> use POR SOR ┨╻┃┍ 1<u>8</u> 2\_L Я i)  $R_T = R_1 + R_2 + R_3$ il In Series current remains constant \* If you add more Resistors in Parallel combined resistance at every point would decrease in Voltage is divided asper resistance.  $\vee \prec R$  $V_{A} = \frac{R_{A}}{x} V_{T}$ R<sub>T</sub> in) If resistance of Any resistor D) Suggest what happenes to Vi increase its corresponding voltage will increase and voltage across and V2 when extra Resistor other resistors will decrease. Z is added in combination.

| ⇒ If there are many Resistors of<br>Some Resistance in parallel<br>(identical) | How to calculate Voltage/<br>Potential at any point<br>in an Electrical circuit |
|--|---|
| $R_{\tau} = \frac{R}{N}$   |   |
| ⇒ Af two constant have Similiant   |   |
| difference blue Here (1000 blue  | A = 102 V   |
| aifference bje them (1000 times  |   |
| be each and land the   | B = 102 - 6 102 - 900   |
| De resistance of Lesser y clue   | 51  |
| 3 $1$ $1$ $1$ $1$ $1$ $1$ $1$ $1$ $1$ $1$                                      |   |
| ) Voltage in Faralle remains Constant  | $\int - \pi t$  |
|  |   |
| 4) Current in parallel gets divided  |   |
| Such that the branch containing  | D= 59   |
| higher resistance gets lesser current  |   |
|  | E = 30  |
|  |   |
|  | F = OV  |
|  | * While moving from a higher potential  |
|  | towards lower potential colculate   |
|  | voltage drop accross each resistor  |
| · · · · · · · · · · · · · · · · · · ·  | and keep on subtracting from  |
|  | previous value  |
|  |   |

Topic:





Topic:

Date:

Kirkhoof DC circuit: \* KCL Kirchoff's law: 62 TI → Purpose: to help us determine the value of current in Electrical 2Л 3 1 circuit involving multiple battries. I? UKCL :- This law states that 22 3 current arriving at a node or **I**2 a junction must be equal to the 1) Label the circuit (CW or ACW) node or junction leaving the node or Junction. 2) Identify the nodes. Node / Junction: refers to any 3) Randomly mark direction in all the branches. and based on point of a circuit where that form an equation for current.  $I_1 + I_2 = I_3$ multiple wires meet or intersect. I1 Note: Every current is Limited to I4 its respective branch extanding from one node to the other node. Form an equation for a current based on KCL Current arriving = Current Leaving  $\boxed{\Box_1 + \Box_2 = \Box_3 + \Box_4}$ \* This Law of KCl is based on low of conservation of charge which states that charge connot be created nor it can be destroyed

Date: Topic: BI A Kirchoff's Voltage Law: (KNL) 2Л <u>3</u> T Consider any closed loop and imagine that you are moving in that loop 1) If you see a battery such that you observe the negative terminal first and then the positive terminal, assume that the voltage is getting raised and write down this voltage as a positive volve. 2) If instead you observe the positive terminal of the battery First and then the negative terminal - while moving in the circuit you assume that the voltage is getting Came across a Resistor then use dropped and write down the rule 3 and 4 Voltage as a negative volue. 3) If your direction of movement \* When you return back to your is the same as the direction Starting pt, equate your equation of current in that branch, then to zero. This law is based on write down voltage of the resistor law of conservation of energy with a negative sign. (ie = -IR) which states that voltage provided 4) If your direction of movement is by the battery is consumed by opposite to the direction of current the resistor in that branch then write down the Sum of voltage in a closed loop voltage with (tve), Sign (ie = +IR) equal to zero.

| Topic:                               | Date: |
|--------------------------------------|-------|
| Note: Solve Simultaneously to        |       |
| Obtain current in each branch.       |       |
| Note: If Incose you get a negative   |       |
| answer for current then this will    |       |
| indicate that the flow of current    |       |
| is popposile to the direction marked |       |
| on the diagram                       |       |
|                                      |       |
| DC circuit                           |       |
| D KCC KVI                            |       |
| 2) Potentiameter                     |       |
|                                      |       |
| Potentiameter                        |       |
|                                      |       |
|                                      |       |
|                                      |       |
|                                      |       |
|                                      |       |
|                                      |       |
|                                      |       |
|                                      |       |
|                                      |       |
|                                      |       |
|                                      |       |
|                                      |       |
|                                      |       |

Topic: Date: \_\_\_\_\_ Potentiometer: A potentiometer Fig**1** 20v (Primary cell) circuit is used to calculate voltage (Unlinown) of power supply 5 25cm-1 R С → How is the circuit constructed and how does it work? Fig1 20v (Primary cell) Seconday cell Q) How much voltage is avalible for the wire AC. Fig 1 shows a resistance wire Voltage across AC = 5V AB connected to a 20v primary cell length of the wire AB Q) For the shaded portion is 100 cm Connecting wire have Zero resistance. of the diagram suggest with a reason, Should the Q) how much Voltage will be availible current flow from Atox For this resistance wire AB or × toA Ans: Current flows from a Ans) 20N (Entire Amount) No other component with Resistance higher potential to a lower potential. It Flows From X to Fl

Topic: Date: \_ How much voltage is avalible across wire of Length AC AC = 3 AB : Voltage across 75cm-1 AC = 154 A B ↑c Hence determine the current 5 in the branch Ax? L Current Flows From A to X 0v JOY What voltage is available for Length AC of the wire AC = 1 AB 101 hence voltage across AC = lov Socm-A R Hence determine the direction of X current in the branch AX 07 Ans:- Null deflection / Zero deflection Why: - Voltage across AC is equal to the voltage of 20V secondary cell. Q) Given that a null deflection/ INDEM A Zerocurrent/Baloncept is a chieved 68 cm 10 В For length AC = G8cm. Use this info to calculate the unknown L Unknown Voltage. voltage of secondary cell.

Topic: Date: \_\_\_ ۷ = 68 x 20 13.62 100 PC = Pimory LAC VPC V = LAB RAC x V= Ver Rag R = Pl  $R \propto 1$ A Q) what is the length of 61 to a chive Null point AC A 180cm, 121 B GOCM 22 61 Calculate the new length of AC 6л now required if an additional 12-2 C A 6\_1 resistor is placed with the primary cell. Step 1 : Find the voltage now available for the length Conclusion: If an extra resistor is placed in the AB using ratio methord.  $V_A = \frac{R_A}{R_T} \times V_T$ primary circuit it causes the length of balance Step 2 : Find length. point to increase.

| Topic:   | Date:  |
|--|--|
| Q) Give an Explaination as to why the length of balance $pt$ has increased i.e. From (60cm $\rightarrow$ 90cm)   |  |
| Ans: If an additional resistor is placed in the primary circuit the voltage now additible for the resistance   |  |
| a much longer length is now required to achive<br>a balance point  |  |
| Q) What happens if 6.0 resistor is replaced by<br>8-0 Resistor ?<br>Step 1 = Colculate Voltage across AB<br>$V_{p} = \frac{R_{0}}{R_{T}} \times \frac{V_{T}}{12+8} \Rightarrow \frac{12}{12+8}$  |  |
| Step 2: $180^{\gamma} \longrightarrow 3.6^{\gamma}$<br>$l \longrightarrow 2^{\gamma}$ $l_{pc} = 100^{cm}$<br>Q) What happens if $6^{\Omega}$ resistor is replaced by<br>30 $\Omega$ resistor.<br>$V_{mirc} = \frac{12}{42} \times 6 \implies 1.7^{\gamma}$<br>$4^{\gamma}$ |  |
| No possibility of achiving balancing point<br>in this case   | Conclusion: - Certain Rules must be kept in mind<br>for a potentiometer circuit to work properly.<br>Rule 1: the terminal of the primary cell must be<br>connected to the the terminal of the secondary cell<br>Rule 2: Voltage of secondary cell has to be be less<br>then or equal to the work property. |

| Topic:  | Date: |
|---|-------|
| 2V<br>I   |       |
|   |       |
|   |       |
|   |       |
| A Extra relitor (2)                                       |       |
| i) In case Ammeter reads zero amperes (null deflection)   |       |
| calculate the unknown voltage V?                          |       |
| $A_{ns}: V_{(ij)} = \frac{4}{4_{+0.5}} \times 2 = 1.78 v$ |       |
| Step 2: 100 1:78  |       |
| $9^{\circ} \longrightarrow y$                             |       |
| V = 1.6 v   |       |
|   |       |
| 1) Suggest Why placing an extra resistor in               |       |
| the secondary circuit as shown will not                   |       |
| hove any effect on the balance point.                     |       |
| ) The term balancing pt indicates that there is zero      |       |
| Current in the secondary circuit. Hence even if you       |       |
| place a resistor, based on V=IR the voltage across        |       |
| this resistor will be V=(0)R ie OV it will not            |       |
| Consume/develope any Voltage across it self hence         |       |
| its pressence or absence cloeonot affect the length       |       |
| of the belonce point.                                     |       |
|   |       |
|   |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |

| Topic: | Date: |
|--------|-------|
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |
|        |       |