Capacitonic = storage capacity. Topic: Capacitance. Date: Capacitor : An electronic device / component that stores electrical Chergy inside it. - It is used to supply extra amount of Energy or charge when Circuit demands. Dielectric (insulator) Symbols Terminal Construction. Working. (Charging) The capacitor is connected to DC a supply . Power 2) The positive terminal of the battery attract electrons from plate A and the -ve terminal deposit them on plate B. 3) This produces a positive charge on plate A and an equal -ve charge on plate B. 4) This deposition of Electrons produces a potential difference across the plates of the copacitor. 5) The greater the charge on plate the higher the voltage induced across them

## Dielectric

Dielectrics are non-conducting materials. It will not have any free-charge carriers.

6) A point comes when charge on plates is enough that potential difference across capacitor gets equal to the EMF of that Battery. The strength with which battery tries to take electrons From A to B becomes equal to the opposition from the capacitor it self. Therefore Charging stops. Completly charged L FWF Completly charged Voltage on capacitor. Current in circuit Working (Discharging) capacitor discharged Electron move from 1) When a -ve to the terminal 2) The current is high at the slant but decreases gradually as the potential difference across falls. After some time PD across capacitor 3) I/A VY is zero + t/s ╋<u></u> Voltage across capacitor Current across copacitor. 🧟 🗍 🛇 0309 2656780 🞯 mahad\_\_amer 🛛 mahadamerchaudhry@gmail.com

Topic: Date: \_\_\_\_ Capacitor Stores energy but not charge why? -After charging both the plates of copacitor achieve equal and opposite charge ► Hence net charge is zero. -> However, work is done in seperating those charges .: energy is stored in the Capacitor. Capacitance: It is the charge stored per unit potential difference on one plate of a capacitor. Stunit = F (Forad) usually we use C = qV = w0NC-9 Define Foral: It is m = Capacitance. the capacitance of the copacitor when IC of charge is stored on one plate «/L of a capacitor for a \* Area = q.V Potential difference of 1vSince V = WO <u>E = 1</u> qV 9xV= WO/Energy. 1 x Vxq  $E = \frac{1}{2} qV$  $\mathcal{E} = \frac{1}{2}(CV)(V)$ 👤 🗋 🕓 0309 2656780 💿 mahad\_\_amer 🛛 mahadamerchaudhry@gmail.com



-			
0	ni	0	
10			۰.

 $Voltage V_{\overline{1}} = V_1 + V_2 + V_3$ The Voltage on each Copacitor depends upon the capacitance, if charge is some Lorge copacitor attains small vallage and Small attains lorge Capacitonce: As q= CV & V= q  $\frac{\Psi_{1}}{C_{1}} + \frac{\Psi_{2}}{C_{2}}$ 9T + 9r3 C3 Сг Ст  $\frac{1}{C_2}$  + Affective copacitore t C3 Ст

-	-			
	0	n	C	۰.
				۰.

Date: \_\_\_\_\_

⇒ Copacitors in Parallel: V.  $\rightarrow$  V<sub>1</sub> = V<sub>2</sub> = V<sub>3</sub> = EMF The Voltage is equal to EMF because Charging Stops when P.D across copacitor is equal to the EMF of source. q = C V ૧ ~ C -> C1 = 100 KF C2 = 50 KF C3 = 150 KF \* 9,3 is more as C3 is largest. \* larger copacitor stores more charge on one plate.  $\rightarrow$   $q_1 + q_2 + q_3 = q_T$ > Battery drives all these electrons from one plate of Copocitors to the next.  $\frac{q}{1} = \frac{q}{1} + \frac{q}{2} + \frac{q}{3}$  $C_{T}V_{T} = C_{1}V_{1} + C_{2}V_{2} + C_{3}V_{2}$   $V_{T} = V(C_{1} + C_{2} + C_{3})$ CT = C1 + C2 + C3 Effective copacilarce.

Topic: Date: GRF GHF GKF 64F  $\bigcirc$ 6 HF  $\frac{1}{CT} = \frac{1}{\kappa} + \frac{1}{\kappa}$ <u>= 3</u> = 2/LF  $\frac{1}{6}$  + 1 > Copocitance of Single coporibor no of copocitors GHF Ст = Сг  $C_{\tau} = 4 \mu_{\rm F}$ CHE CRE GRE 34F + 6RF = 94F Uses of capacitors. 4) Rectifiers (Converting AC to DC) 1- Stores energy 2- Stabilizers 3 - Tuning circuits. 30/LF, 6V mcx. A Mox of 6V can be applied A Voltage above 6V across the Capacitor and would cause insulation of conbechaged to a Copacitor to fail which maximum of 6V leads to discharging.

Topic: Date: \_\_\_\_\_ V2  $\sqrt{.}$ 60 JEF UO RF  $C_1 = 40 HF_2 6 Vmax$ C2 - GORF, 6Vmax What is the safest Voltage that Can be applied across the combination. Vr = )  $V_{\Gamma} = V_{1} + V_{2}$  $V_T = V_1 + \frac{2}{3}V_1$ Since charge is some on q = q  $C_1 V_1 = C_2 V_2$ 40 V, - 60 V,  $V_{\Gamma} = G + \frac{2}{3} \left( 6 \right)$  $\frac{40}{60}V_{1} = V_{2}$  $V_{F} = 10 v$ 

Date:			

Chorging	one C	apacitor usin	g another	copacitor.
			herged	
		<u> </u>		
		> lun	charged.	
* Canacitors	are attache	l in Dara	let to e	one another.
* Electrons	move from	One Cope	acitor to	the next.
* The Charge	& copacito	r now dis	charges on	d uncharged one gets
charged.				
+ The process	stops w	hen both	the CODO	citors achive. the
Some P.	o (v of	2 the one	capacitor	falls as it discharges
and other	Canacitar	V rises a	s it cha	( <i>ae</i> 2)
Initial Enc	ryy Find	Energy		
$E = 1 (\gamma)^2$	J	- J >	Consilar	
2	E = _	$\frac{1}{C_{T}}$ $V_{T}$	$C_{T} = C_{1} +$	$C_1$
		$z = C_T V_T$		
		$q = V_T$		
YOUF	aged	Cr		
	<u> </u>	i) q.		ii) CT
	Choraed	jii) VT		iv) A.E
604F V1 = 6V	- ]=)			,

Topic:



$\begin{array}{c} \mathbf{q} & \mathbf{t} \\ \mathbf{q} & \mathbf{t} \\ \mathbf{t} \end{array}$	$C = \frac{q}{N}$
	C = <u>%</u>
	R R
	C = R
	<u>Ι</u> <u>Ψτε</u> ,
R	- */m
	$C = 4\pi E_0 R$
e capaciton depend	upon the radius of the
sphere.	

## 16. M/J 08/P4/Q5

A capacitor C is charged using a supply of e.m.f. 8.0V. It is then discharged through a resistor R.

The circuit is shown in Fig. 5.1.



The variation with time t of the potential difference V across the resistor R during the discharge of the capacitor is shown in Fig. 5.2.



(a) During the first 1.0s of the discharge of the capacitor, 0.13J of energy is transferred to the resistor R.

Show that the capacitance of the capacitor C is 4500 µF.



(b) Some capacitors, each of capacitance 4500 µF with a maximum working voltage of 6V, are available.

Draw an arrangement of these capacitors that could provide a total capacitance of 4500 µF for use in the circuit of Fig. 5.1.

[2]

[3]

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Topic:	Date:

Торіс:	Date:

Торіс:	Date:

Торіс:	Date:

Торіс:	Date:

Торіс:	Date:

Торіс:	Date:

Торіс:	Date: